## Lesson Outline

## Electric Current and Simple Circuits

- **A.** Electric Current and Electric Circuits
  - **1.** A(n) \_\_\_\_\_\_ is the movement of electrically charged particles.
  - **2.** An electric current can flow in a(n) \_\_\_\_\_\_ path to and from a source of electric energy.
    - **a.** A(n) \_\_\_\_\_\_ is a closed path in which an electric current travels.
    - **b.** If the circuit is broken, or \_\_\_\_\_\_, then electrons do not flow.
  - **3.** The number of electrons leaving a power source \_\_\_\_\_\_ the number of electrons entering it.
  - **4.** Electrons are counted using a unit called the \_\_\_\_\_\_.
    - a. The SI unit for electric current is the \_\_\_\_\_\_.
    - **b.** An ampere is about 1 \_\_\_\_\_\_ of electrons flowing past
      - a point in a circuit every \_\_\_\_\_.

## **B.** What is electrical resistance?

- **1.** \_\_\_\_\_\_ is a measure of how difficult it is for an electric current to flow in a material.
- **2.** The unit of electric resistance is the \_\_\_\_\_\_.
- **3.** A good conductor has \_\_\_\_\_\_\_ electric resistance, and a good insulator has \_\_\_\_\_\_\_ electric resistance.
- **4.** Electric resistance depends on the \_\_\_\_\_\_ and the thickness of the material.
  - **a.** When the thickness of a conductor increases, its electric resistance \_\_\_\_\_\_.
  - **b.** When the length of a conductor increases, its electric

| resistance |  |
|------------|--|
|            |  |

30

## **Lesson Outline continued**

D. Ohm's Law

| 1. | The and the resistance of a circuit are related. When                            |
|----|--|
|    | the resistance of a circuit increases, the current in the                        |
|    | circuit  |
| 2. | is a mathematical equation that describes the                                    |
|    | relationship among, current, and   |
|    | <b>a.</b> According to Ohm's law, voltage equals times resistance.               |
|    | <b>b.</b> When using Ohm's law, voltage has units of, current                    |
|    | has units of, and resistance has units   |
|    | of   |
| 3. | When current is constant, devices that have resistance use more electric energy. |

Electricity