

Lesson Outline**LESSON 3*****Describing Circuits*****A. Parts of an Electric Circuit**

1. An electric circuit transforms _____ energy to other forms of energy.
2. An electric circuit contains a(n) _____ source.
 - a. A(n) _____ is often used as an energy source.
 - b. As chemicals react within a battery, the battery's _____ terminal loses electrons and its _____ terminal gains electrons.
 - c. When the terminals are connected in a closed circuit, electrons flow from the _____ terminal of a battery to the _____ terminal.
3. An electric circuit contains at least one electric _____ that transforms energy.
 - a. Within a battery, _____ energy transforms into _____ energy of moving electrons.
 - b. When the electrons flowing in a conductor _____ with the atoms that make up the conductor, the electrons transfer some of their _____ energy to the atoms.
4. An electric circuit contains _____ that connect its components.
 - a. Wires that connect components of a circuit have _____ electric resistance.
 - b. Only a small amount of electric energy is transformed into _____ energy by wires, which means that more energy is available for useful devices in the circuit.

B. Series and Parallel Circuits

1. A(n) _____ circuit is an electric circuit that has only one closed path for an electric current to follow.
 - a. Because there is only one path, when a series circuit is _____, all _____ turn off.

Lesson Outline continued

- b.** Adding devices to a series circuit adds _____ to the circuit and _____ the current in the circuit.
- 2.** A(n) _____ circuit is an electric circuit that has more than one closed path for an electric current to follow.
- a.** Most circuits in homes are _____ circuits.
- b.** In a parallel circuit, each _____ has its own path, or _____, that connects it to the source.
- c.** If you _____ one branch of a parallel circuit, current continues through other branches.
- d.** Adding devices and branches to a parallel circuit _____ the total electric current through the _____.
- C. Electric Circuits in the Home**
- 1.** Electric energy is generated at large _____.
- 2.** Before entering your house through a main _____, the main wire passes through a(n) _____, which measures the _____ used in your home.
- 3.** _____ and circuit _____ are safety devices that keep the _____ in a circuit from becoming too high.
- 4.** A(n) _____ is a safety device in an electric outlet that opens a circuit to stop current flow, which can help protect you from electric _____.
- D. Electric Safety**
- 1.** An electric shock occurs when a(n) _____ passes through the _____.
- 2.** Ways to protect yourself from electric shock include staying away from _____ while using electric devices, avoiding using _____ cords, and not contacting electric power _____.