

School to Home

LESSON 3

Describing Circuits

Directions: Use your textbook to complete the activity.

1. Fill in the Venn diagram to compare and contrast series circuits and parallel circuits. Place each of the phrases in the word bank in the correct part of the diagram.

Adding devices reduces current.

Adding devices increases current through the battery.

If one device is broken, the current stops flowing.


more than one path for current

one path for current

used for most household devices

uses a source of electric energy

uses wires to carry current

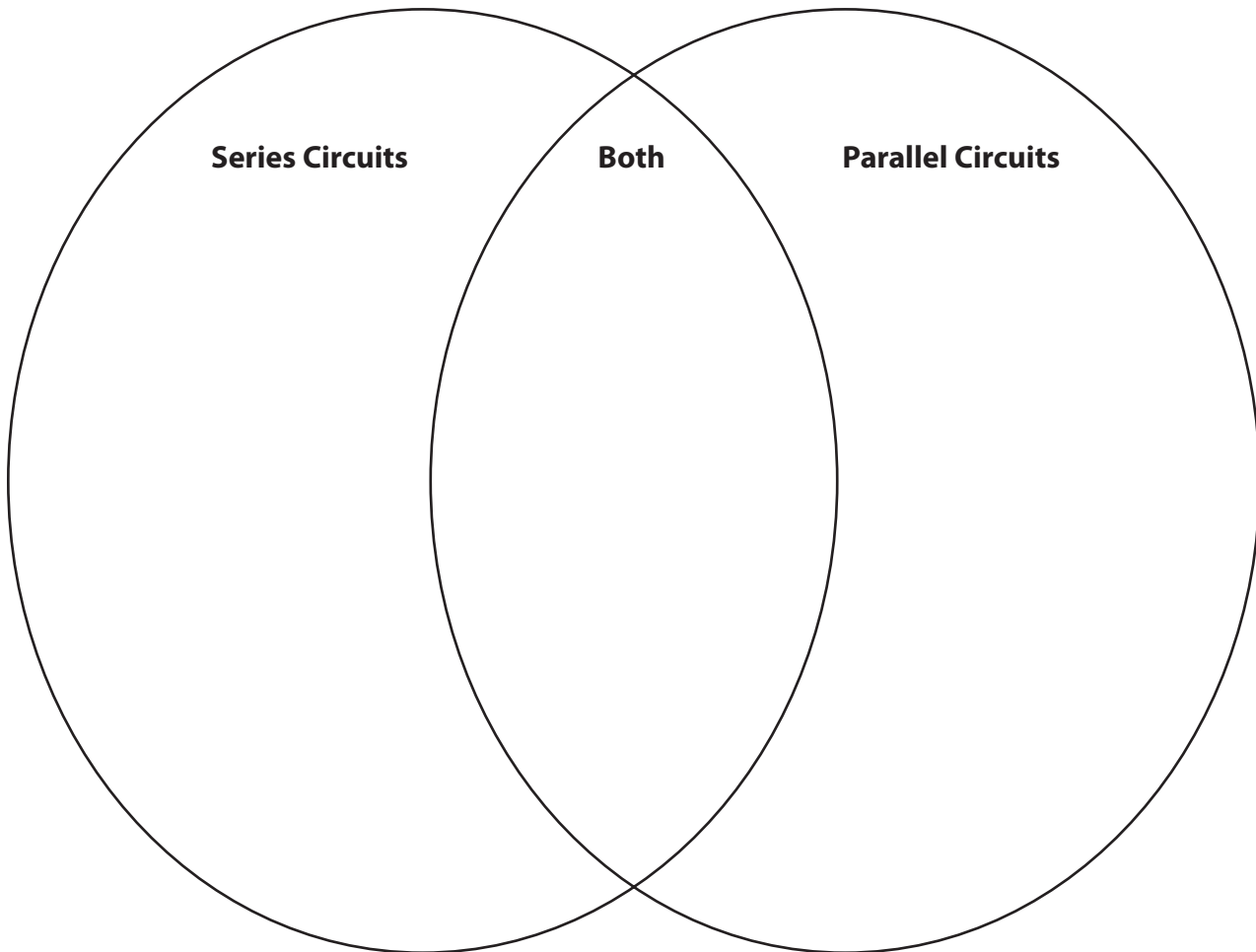

Copyright © Glencoe/McGraw-Hill, a division of The McGraw-Hill Companies, Inc.